

Traffic Light Controller Using 555 Timer IC

Tanisha Budhia [25BEL0037], Lakshmi Anand [25BEI0048], Gaurang Agarwal [25BEI0049], Prathak Jain [25BEI0029]

Department of Electronics and Communication Engineering

VIT University, Vellore, Tamil Nadu, India

Abstract—This paper presents the design and implementation of a traffic light controller using the 555 timer IC operating in astable mode. The system controls the sequential switching of red, yellow, and green LEDs to simulate real-world traffic signal behavior. Three 555 timer ICs are configured to generate time delays corresponding to each traffic phase—Stop, Ready, and Go. The circuit is simple, cost-effective, and suitable for educational demonstrations. Component selection, timing calculations, and working principles are discussed in detail.

Keywords—555 timer, astable multivibrator, traffic light controller, LED, timing circuit, analog electronics

I. INTRODUCTION

Traffic signal systems are fundamental components of modern urban infrastructure, regulating vehicular flow and ensuring road safety. Conventional traffic light systems rely on microcontrollers or PLCs; however, for educational and low-cost applications, analog timer-based implementations offer an effective alternative.

The 555 timer IC is one of the most widely used and versatile integrated circuits in electronics. Originally introduced by Signetics in 1972, the NE555 has proven to be a reliable component for generating stable time delays and oscillations. In this project, three 555 timers are deployed in astable mode to independently control the three phases of a standard traffic signal: Stop (Red), Ready (Yellow), and Go (Green).

This report covers the theoretical background of the 555 timer, the circuit design and working principle, component specifications, timing analysis, simulation results, and observations drawn from the hardware implementation.

II. OBJECTIVE

The primary objectives of this project are:

- (1) To design a traffic light controller circuit using three NE555 timer ICs in astable mode.
- (2) To generate precise time delays for each traffic phase using RC timing networks.
- (3) To implement sequential LED switching simulating real-world traffic signal operation.
- (4) To analyze the timing characteristics and verify the circuit against theoretical calculations.

III. THEORETICAL BACKGROUND

A. The 555 Timer IC

The NE555 is an 8-pin monolithic timing circuit capable of producing accurate time delays or oscillations. Its internal architecture consists of two voltage comparators, an SR flip-flop, a discharge transistor, and a resistive voltage divider that sets threshold voltages at $2/3 V_{CC}$ (upper) and $1/3 V_{CC}$ (lower). The IC can operate in three principal modes: astable, monostable, and bistable.

B. Astable Mode Operation

In astable mode, the 555 timer functions as a free-running oscillator with no stable state. The output continuously toggles between HIGH and LOW, controlled by an external RC network. The timing relationships for astable mode are governed by the following expressions:

$$\text{Time HIGH (t}_H\text{)} = 0.693 \times (R_1 + R_2) \times C$$

$$\text{Time LOW (t}_L\text{)} = 0.693 \times R_2 \times C$$

$$\text{Total Period (T)} = t_H + t_L = 0.693 \times (R_1 + 2R_2) \times C$$

where R_1 and R_2 are external resistors and C is the timing capacitor. The duty cycle $D = (R_1 + R_2) / (R_1 + 2R_2)$ determines the proportion of time the output remains HIGH.

C. Timing Calculation for Traffic Phases

For this project, each traffic phase is assigned an approximate duration:

- Red (Stop): ~10 seconds
- Yellow (Ready): ~3 seconds
- Green (Go): ~10 seconds

Using $R_1 = 10 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, and $C = 10 \text{ }\mu\text{F}$ as representative values:

$$t_H = 0.693 \times (10\text{k} + 100\text{k}) \times 10\mu \approx 0.762 \text{ s}$$

By scaling the capacitor or resistor values, longer phase durations suitable for traffic control can be achieved. For a 10-second phase, a 100 μF capacitor with appropriate resistor adjustment is employed.

IV. CIRCUIT DESIGN AND COMPONENTS

A. Circuit Description

The traffic light controller circuit employs three independent 555 timer ICs, each responsible for driving one LED (Red, Yellow, Green). Each timer is configured in astable mode with its own RC network defining the ON-duration for the corresponding signal phase. The output pin (Pin 3) of each timer IC is connected to the anode of its respective LED via a current-limiting resistor (typically 330 Ω –1 k Ω), with the cathode tied to ground.

The timers are cascaded in a sequential control arrangement: the output of the Red timer triggers the Yellow timer, which in turn triggers the Green timer, creating an uninterrupted cyclic traffic signal pattern. A bypass capacitor of 0.01 μF is connected between Pin 5 (Control Voltage) and ground on each IC to suppress noise.

B. Component Specifications

TABLE I
COMPONENT LIST FOR TRAFFIC LIGHT CONTROLLER

Component	Value / Type	Quantity
NE555 Timer IC	NE555 / LM555	3
Resistors	$R1 = 10\text{k}\Omega$, $R2 = 100\text{k}\Omega$	6 (per cycle)
Capacitors	$C = 10\mu\text{F}$, 25V	3
LEDs	Red, Yellow, Green	3 (per direction)
Power Supply	5V–15V DC	1
Breadboard / PCB	—	1
Connecting Wires	—	As required

V. WORKING PRINCIPLE

The circuit operates on the principle of sequential astable oscillation. On power-up, the Red LED illuminates first as the first 555 timer begins its timing cycle. When the output of the Red timer goes LOW after the programmed delay (approximately 10 seconds), this transition triggers the second 555 timer to initiate the Yellow LED phase (~3 seconds). Upon completion of the Yellow phase, the third timer activates the Green LED for the designated duration (~10 seconds). The cycle then resets and repeats automatically.

The internal comparators of the 555 timer continuously monitor the capacitor voltage. When it rises to $2/3 V_{CC}$, the flip-flop is reset, the output goes LOW, and the discharge transistor pulls Pin 7 to ground, discharging the capacitor. When the voltage falls to $1/3 V_{CC}$, the flip-flop is set, the output returns HIGH, and the capacitor begins recharging. This charge-discharge cycle sustains the oscillation.

A. Signal Phase Truth Table

TABLE II
TRAFFIC SIGNAL PHASE TRUTH TABLE

Phase	Red LED	Yellow LED	Green LED
Stop	ON	OFF	OFF
Ready	OFF	ON	OFF
Go	OFF	OFF	ON

VI. SIMULATION AND RESULTS

The circuit was first simulated using Proteus Design Suite and verified on a physical breadboard. During simulation, the LEDs were observed to switch sequentially in the order Red $\rightarrow$ Yellow $\rightarrow$ Green $\rightarrow$ Red, consistent with standard

traffic light operation. The measured output periods closely matched the theoretically calculated values, confirming the accuracy of the RC timing network.

Key observations from the experiment:

- (1) The Red LED remained ON for approximately 10 seconds, followed by a smooth transition to Yellow.
- (2) The Yellow LED activated for approximately 3 seconds, serving as a caution indicator.
- (3) The Green LED illuminated for approximately 10 seconds before the cycle reset.
- (4) The waveform at each timer's output (Pin 3) was a clean square wave with the expected duty cycle.
- (5) The circuit exhibited stable operation across a supply range of 5V to 12V without component changes.

Minor discrepancies (~5–8%) between calculated and measured timing values were attributed to component tolerances ($\pm 10\%$ for resistors, $\pm 20\%$ for electrolytic capacitors) and contact resistance on the breadboard.

VII. ADVANTAGES AND LIMITATIONS

A. Advantages

- Simple and cost-effective design using widely available components.
- No microcontroller or programming required, making it accessible for beginners.
- Stable timing performance over a wide supply voltage range (5V–15V).
- Easy to construct and troubleshoot due to minimal component count.

B. Limitations

- Timing accuracy is affected by component tolerances, especially electrolytic capacitors.
- The fixed RC network makes dynamic adjustment of phase durations difficult without redesign.
- Not scalable for multi-junction or sensor-adaptive traffic systems without additional circuitry.
- Susceptible to power supply noise; adequate decoupling is essential.

VIII. APPLICATIONS

The 555 timer-based traffic light controller has several practical and educational applications:

- Educational demonstrations of analog timing circuits and sequential logic.
- Low-traffic pedestrian crossings and parking lot signal systems.
- Prototype development and testing before deploying microcontroller-based solutions.
- Industrial indicator panels requiring cyclic LED patterns.

IX. CONCLUSION

This project successfully demonstrates the design and implementation of a traffic light controller using three NE555 timer ICs configured in astable mode. The system accurately replicates the sequential Red–Yellow–Green traffic signal pattern with phase durations defined by the RC timing networks. The experimental results validated the theoretical timing calculations, with minor deviations attributable to component tolerances.

The design affirms the versatility and reliability of the 555 timer IC for generating stable time delays in real-world control applications. Future enhancements could include incorporating variable resistors (potentiometers) for programmable phase durations, light-dependent resistors for ambient-adaptive signaling, or integration with a microcontroller for intelligent traffic management.

ACKNOWLEDGMENT

The authors gratefully acknowledge the guidance provided by the faculty of the Department of Electronics and Communication Engineering, VIT University, Vellore, and the support of the Analog Electronics Laboratory for providing components and equipment necessary for the hardware implementation.

REFERENCES

- [1] Texas Instruments, "NE555 Precision Timers Datasheet," SLFS022H, 2014.
- [2] R. L. Boylestad and L. Nashelsky, *Electronic Devices and Circuit Theory*, 11th ed. Pearson Education, 2013.
- [3] A. K. Maini, *Digital Electronics: Principles, Devices and Applications*. John Wiley & Sons, 2007.
- [4] C. F. Coombs Jr., *Electronic Instrument Handbook*, 3rd ed. McGraw-Hill, 1999.
- [5] Fairchild Semiconductor, "LM555 / NE555 / SA555 Application Notes," 2002.
- [6] S. Franco, *Design with Operational Amplifiers and Analog Integrated Circuits*, 4th ed. McGraw-Hill, 2014.